

Scilab Manual for
Basic Analog VLSI lab
by Dr Sandhya Save
Electronics Engineering
University of Mumbai¹

Solutions provided by
Dr Dr. Sandhya Save
Electronics Engineering
University of Mumbai

June 19, 2026

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Scilab Manual and Scilab codes written in it can be downloaded from the "Migrated Labs" section at the website <http://scilab.in>

Contents

List of Scilab Solutions	3
1 CMOS Inverter Amplifier	5
2 CMOS transmission gate	7
3 NMOS current mirror circuit	9
4 NMOS Cascode current mirror circuit	11
5 NMOS Wilson current mirror circuit	13

List of Experiments

List of Figures

1.1	CMOS inverter	6
1.2	CMOS inverter	6
2.1	CMOS transmission gate	8
2.2	CMOS transmission gate	8
3.1	Basic current mirror circuit	10
3.2	Basic current mirror circuit	10
4.1	Cascode current source	12
4.2	Cascode current source	12
5.1	Wilson current mirror	14
5.2	Wilson current mirror	14

Experiment: 1

CMOS Inverter Amplifier

This code can be downloaded from the website www.scilab.in

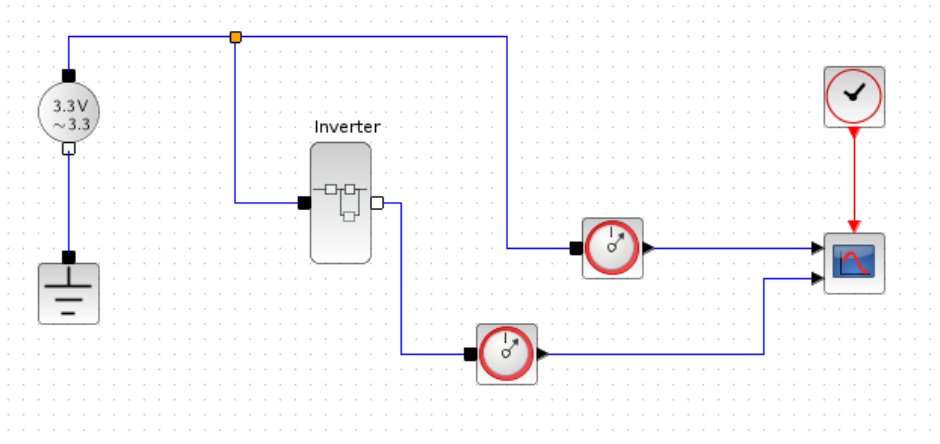


Figure 1.1: CMOS inverter

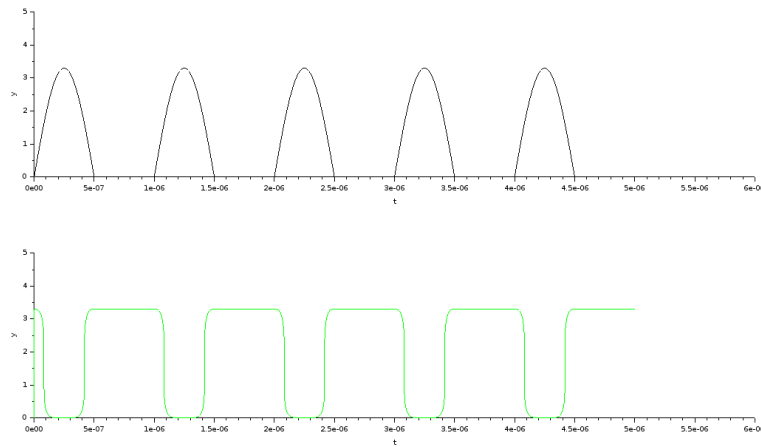


Figure 1.2: CMOS inverter

Experiment: 2

CMOS transmission gate

This code can be downloaded from the website www.scilab.in

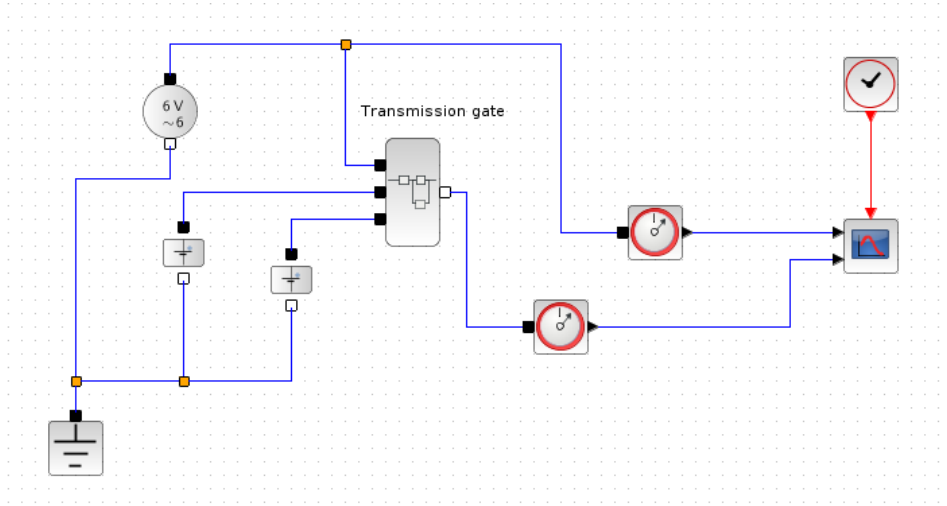


Figure 2.1: CMOS transmission gate

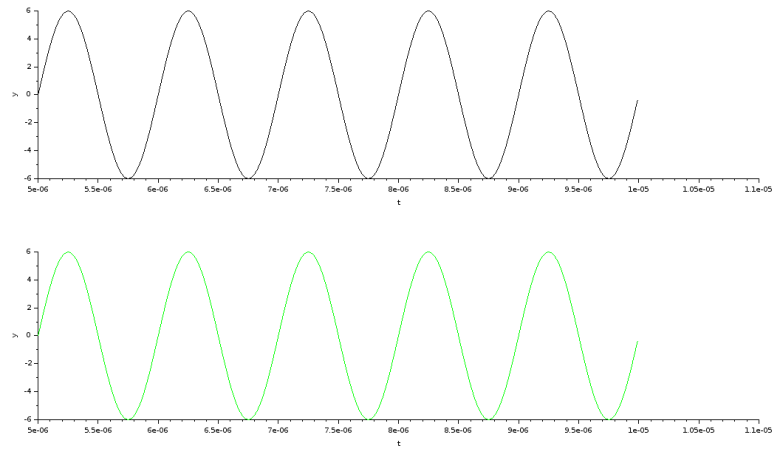


Figure 2.2: CMOS transmission gate

Experiment: 3

NMOS current mirror circuit

This code can be downloaded from the website www.scilab.in

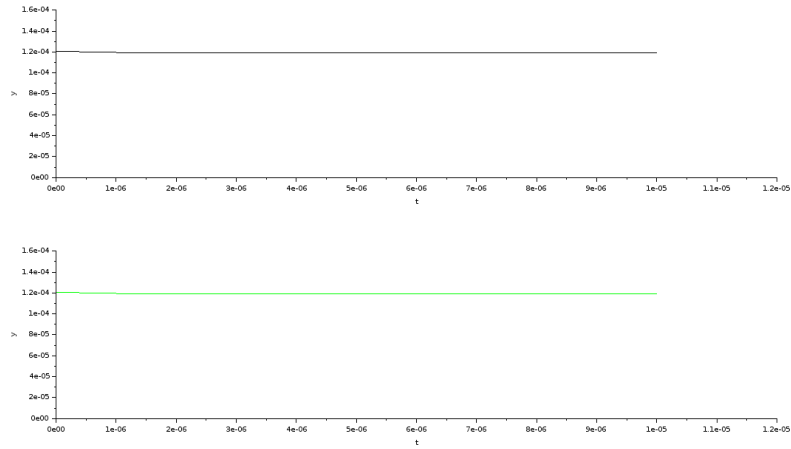


Figure 3.1: Basic current mirror circuit

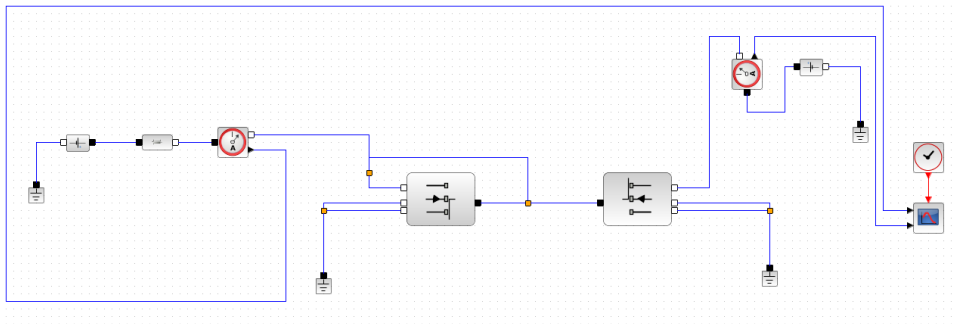


Figure 3.2: Basic current mirror circuit

Experiment: 4

NMOS Cascode current mirror circuit

This code can be downloaded from the website www.scilab.in

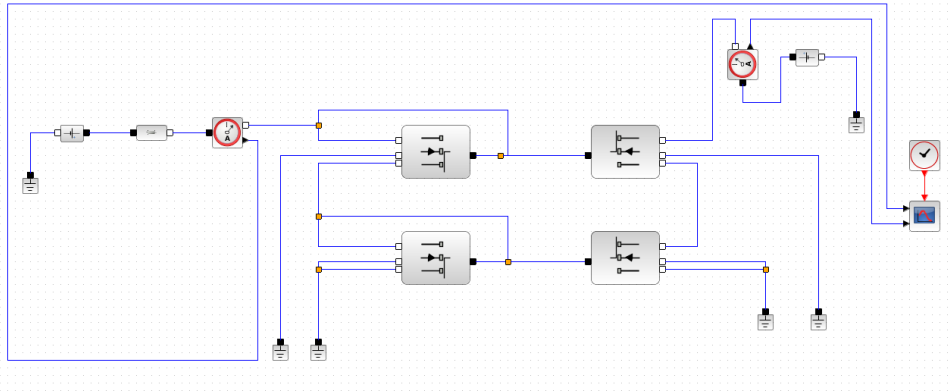


Figure 4.1: Cascode current source

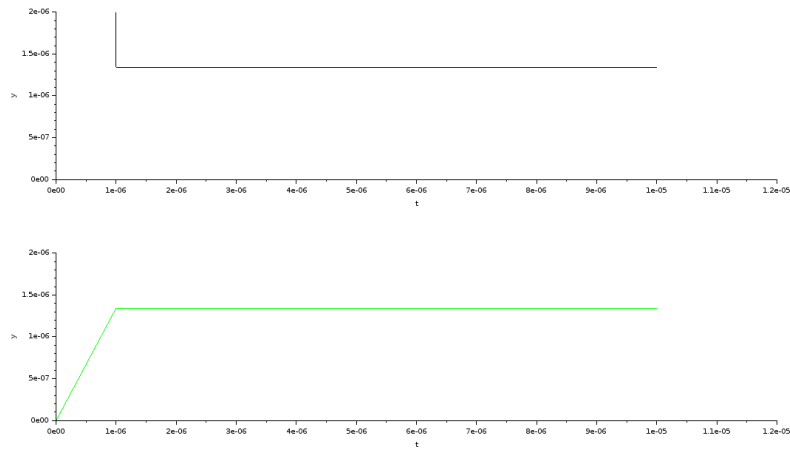


Figure 4.2: Cascode current source

Experiment: 5

NMOS Wilson current mirror circuit

This code can be downloaded from the website www.scilab.in

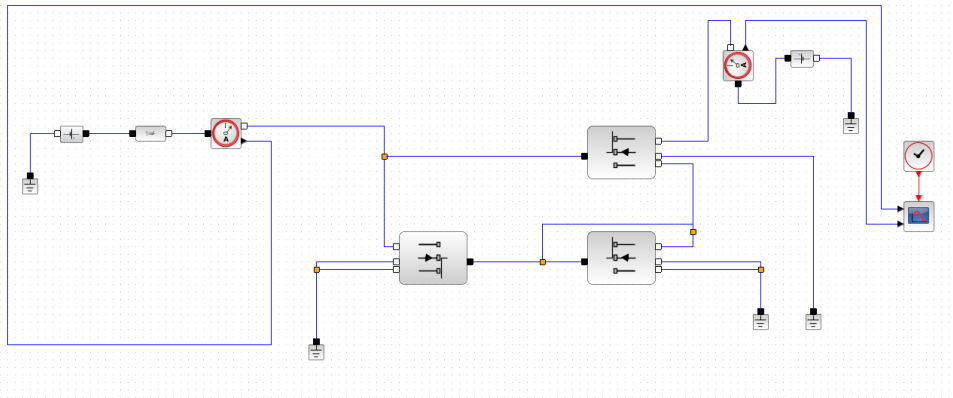


Figure 5.1: Wilson current mirror

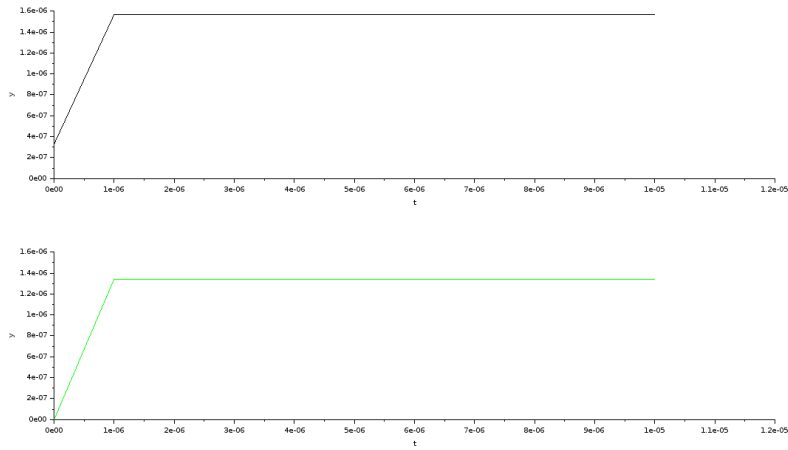


Figure 5.2: Wilson current mirror