

Scilab Manual for  
Simulation lab / Pulse & Digital Circuits lab /  
SEEK Course (Skill for Employability  
Enhancement of Knowledge) / DLDMP lab  
by Dr Jitesh Ramdas Shinde  
Others  
Vaagdevi College Of Engineering<sup>1</sup>

Solutions provided by  
Dr Jitesh Ramdas Shinde  
Others  
Vaagdevi College Of Engineering

April 2, 2026

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Scilab Manual and Scilab codes written in it can be downloaded from the "Migrated Labs" section at the website <http://scilab.in>



# Contents

List of Scilab Solutions	4
1 Digital Logic Gates Design & Implementation in Xcos	7
2 Half Adder and Full Adder Design & Implementation in Xcos	11
3 Half Subtractor and Full Subtractor Design & Implementation in Xcos	14
4 4 bit Ripple Carry Adder Design & Implementation in Xcos	17
5 BCD Adder Design & Implementation in Xcos	20
6 Multiplexer Design and implementation & its application in Xcos	22
7 Demultiplexer Design and implementation & its application in Xcos	25
8 Decoder Design and implementation & its application in Xcos	28
9 Flip flop Design & Implementation in Xcos	31
10 Asynchronous Counter Design & Implementation in Xcos	34
11 Synchronous Counter Design & Implementation in Xcos	36

12 Code Converter Design (eg.binary to gray code conversion)  
& Implementation in Xcos

39

# List of Experiments

# List of Figures

1.1	XOR gate design using basic logic gates . . . . .	8
1.2	XOR gate design using basic logic gates . . . . .	8
1.3	XOR gate design using NAND gate . . . . .	9
1.4	XOR gate design using NAND gate . . . . .	9
1.5	XOR gate design using NOR gate . . . . .	10
1.6	XOR gate design using NOR gate . . . . .	10
2.1	Half Adder design . . . . .	12
2.2	Half Adder design . . . . .	12
2.3	Full Adder Design . . . . .	13
2.4	Full Adder Design . . . . .	13
3.1	Half Subtractor design . . . . .	15
3.2	Half Subtractor design . . . . .	15
3.3	Full Subtractor Design . . . . .	16
3.4	Full Subtractor Design . . . . .	16
4.1	Ripple Carry Adder Design . . . . .	18
4.2	Ripple Carry Adder Design . . . . .	19
4.3	Ripple Carry Adder Design . . . . .	19
5.1	BCD Adder Design . . . . .	21
5.2	BCD Adder Design . . . . .	21
6.1	Multiplexer 4 to 1 design . . . . .	23
6.2	Multiplexer 4 to 1 design . . . . .	23
6.3	Multiplexer Application Half Adder design . . . . .	24
6.4	Multiplexer Application Half Adder design . . . . .	24
7.1	Demultiplexer 1 to 4 . . . . .	26

7.2	Demultiplexer 1 to 4 . . . . .	26
7.3	Demultiplexer Application Half Adder design . . . . .	27
7.4	Demultiplexer Application Half Adder design . . . . .	27
8.1	Decoder 2 to 4 design . . . . .	29
8.2	Decoder 2 to 4 design . . . . .	29
8.3	Decoder Application Half Subtractor design . . . . .	30
8.4	Decoder Application Half Subtractor design . . . . .	30
9.1	JK flip flop . . . . .	32
9.2	JK flip flop . . . . .	32
9.3	D flip flop . . . . .	33
9.4	D flip flop . . . . .	33
10.1	Asynchronous 3 bit up counter design . . . . .	35
10.2	Asynchronous 3 bit up counter design . . . . .	35
11.1	Three bit up synchronous counter . . . . .	37
11.2	Three bit up synchronous counter . . . . .	37
11.3	Three bit down synchronous counter . . . . .	38
11.4	Three bit down synchronous counter . . . . .	38
12.1	Binary to Gray code converter . . . . .	40
12.2	Binary to Gray code converter . . . . .	41
12.3	Binary to Gray code converter . . . . .	42
12.4	Binary to Gray code converter . . . . .	42

# Experiment: 1

## Digital Logic Gates Design & Implementation in Xcos

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

*EX-OR Gate Implementation using Basic Logic Gates*

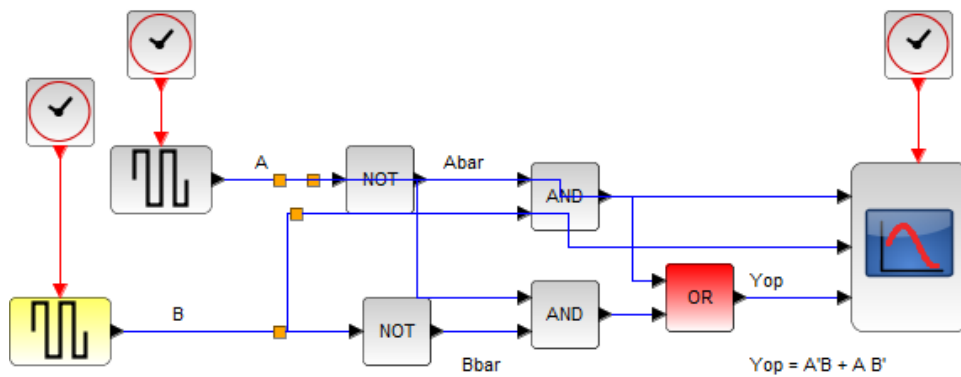


Figure 1.1: XOR gate design using basic logic gates

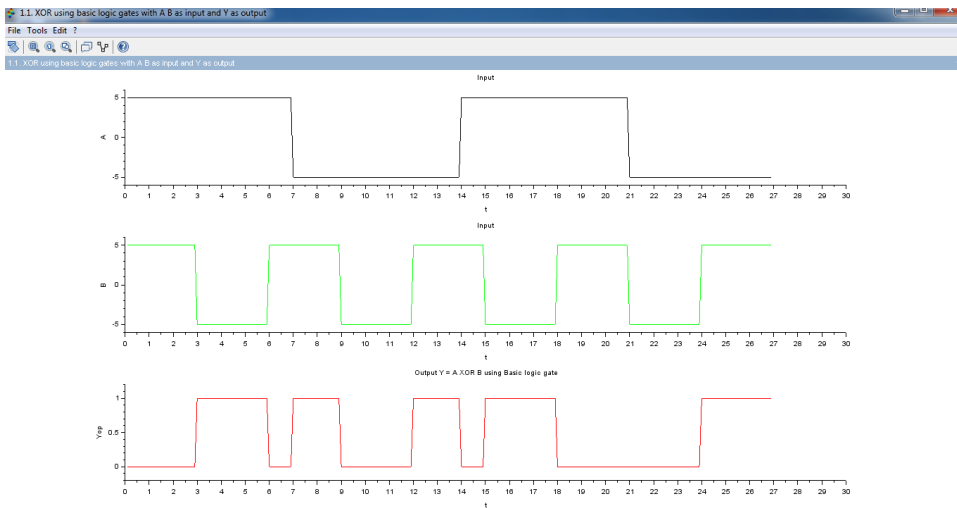


Figure 1.2: XOR gate design using basic logic gates

*EX-OR Gate Implementation using Universal Logic Gate NAND only*

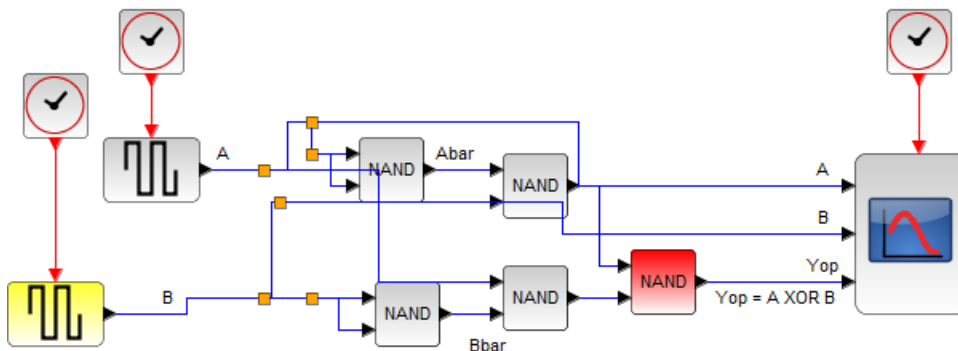


Figure 1.3: XOR gate design using NAND gate

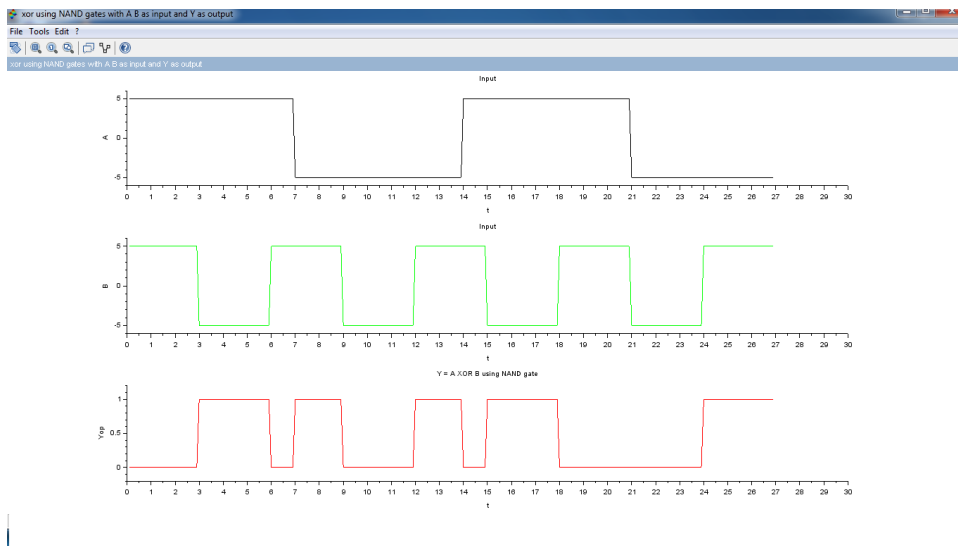


Figure 1.4: XOR gate design using NAND gate

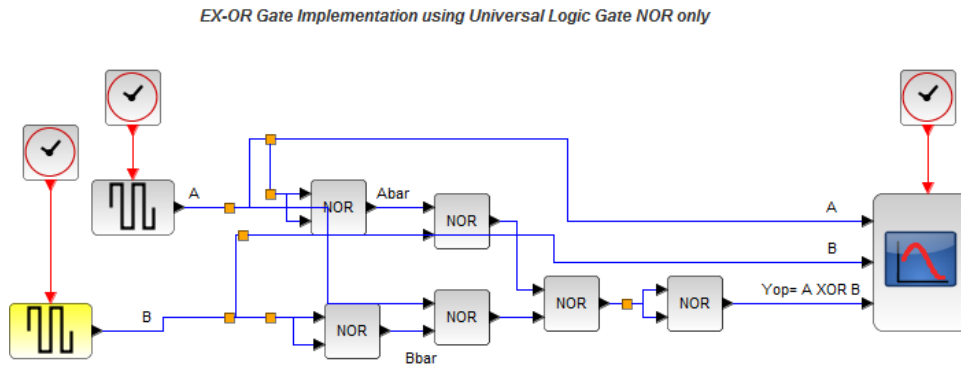


Figure 1.5: XOR gate design using NOR gate

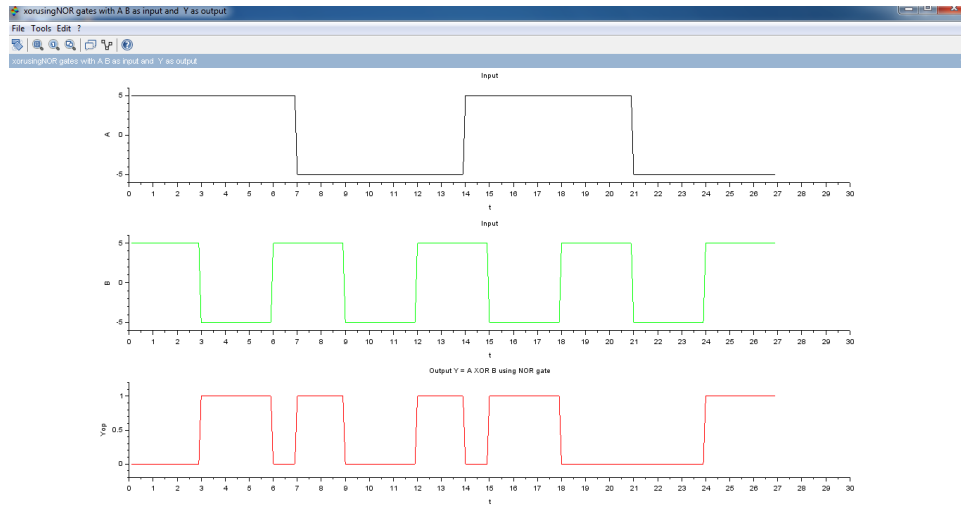


Figure 1.6: XOR gate design using NOR gate

## **Experiment: 2**

# **Half Adder and Full Adder Design & Implementation in Xcos**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

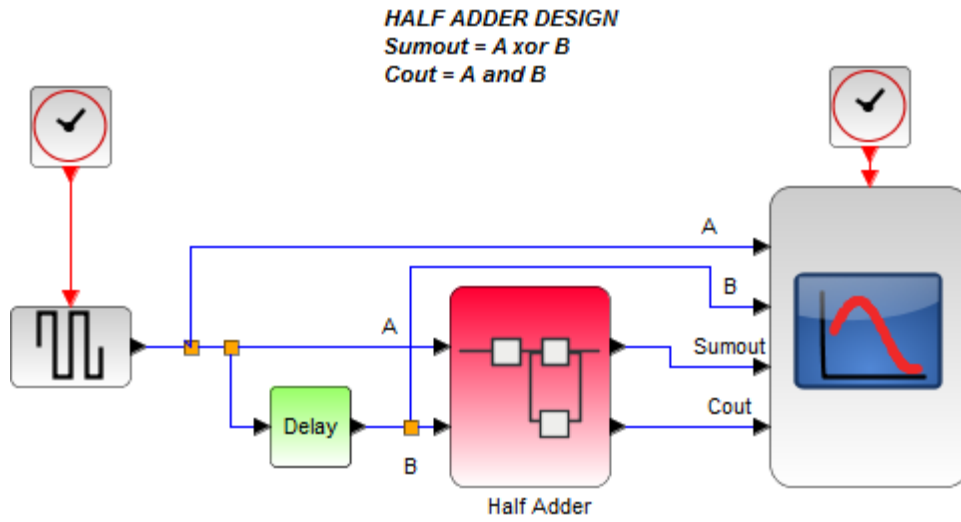


Figure 2.1: Half Adder design


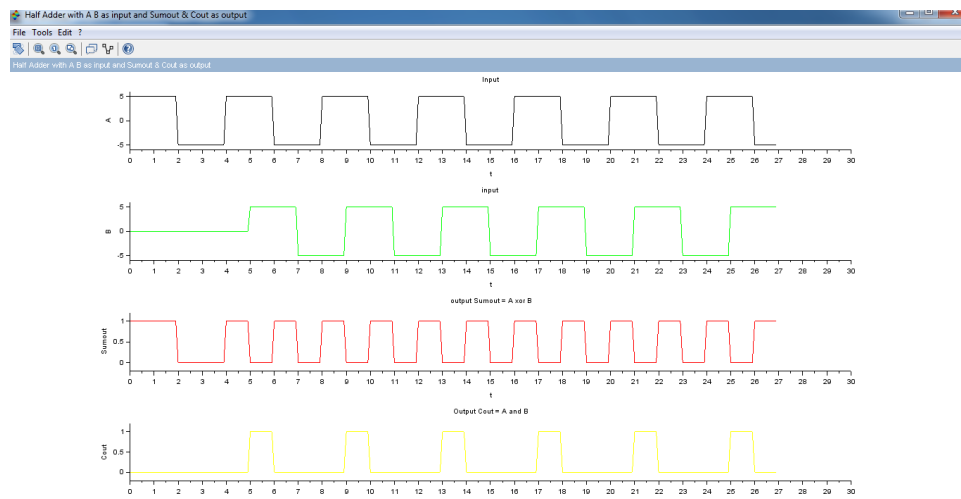


Figure 2.2: Half Adder design

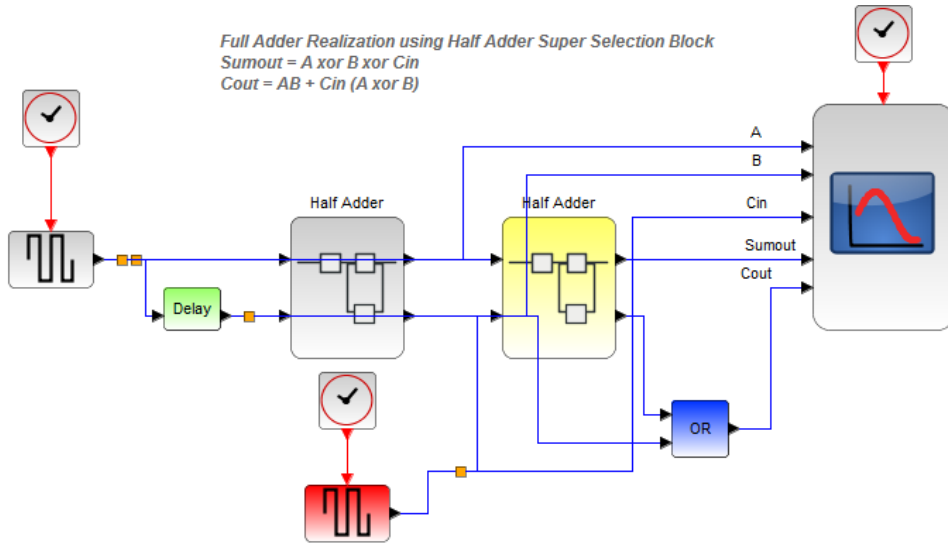

Note : Superselection of superselection not supported in Scilab Xcos.

Figure 2.3: Full Adder Design

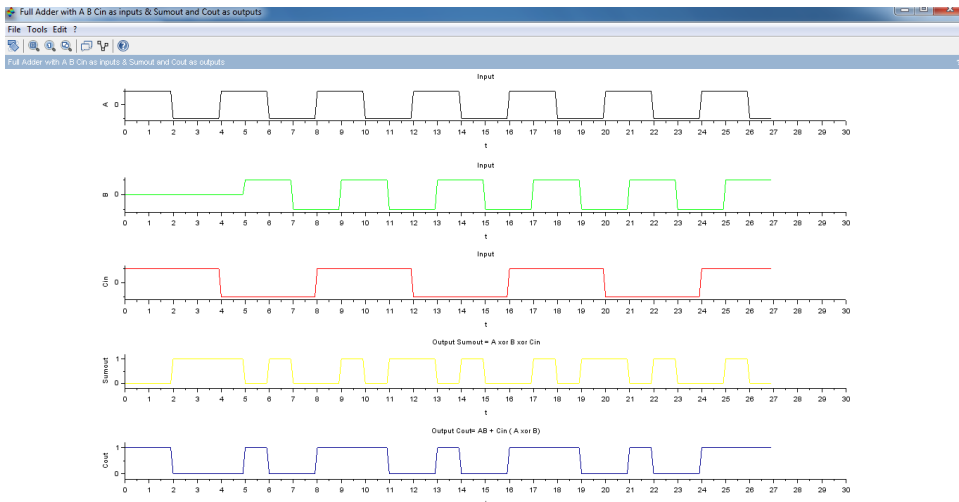


Figure 2.4: Full Adder Design

## **Experiment: 3**

# **Half Subtractor and Full Subtractor Design & Implementation in Xcos**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

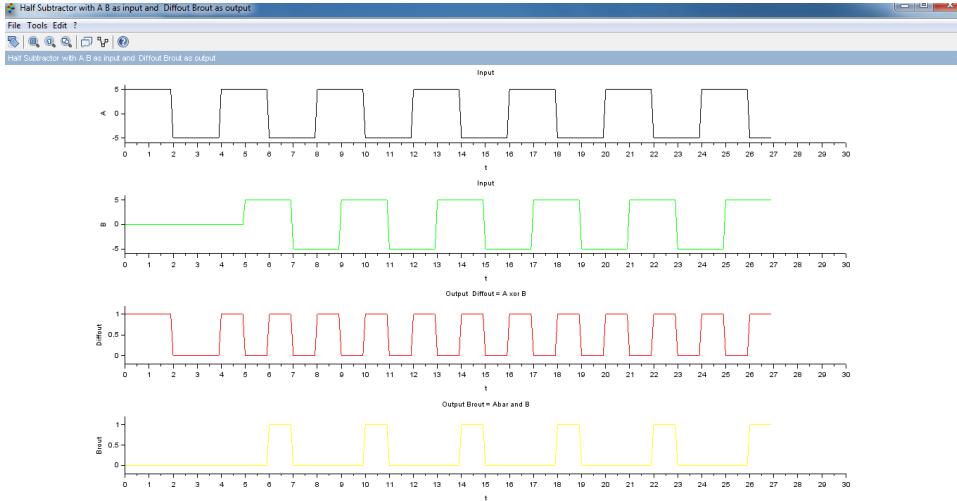


Figure 3.1: Half Subtractor design

**Half Subtractor Design**  
 $Diffout = A \text{ xor } B$   
 $BrouT = A' B$


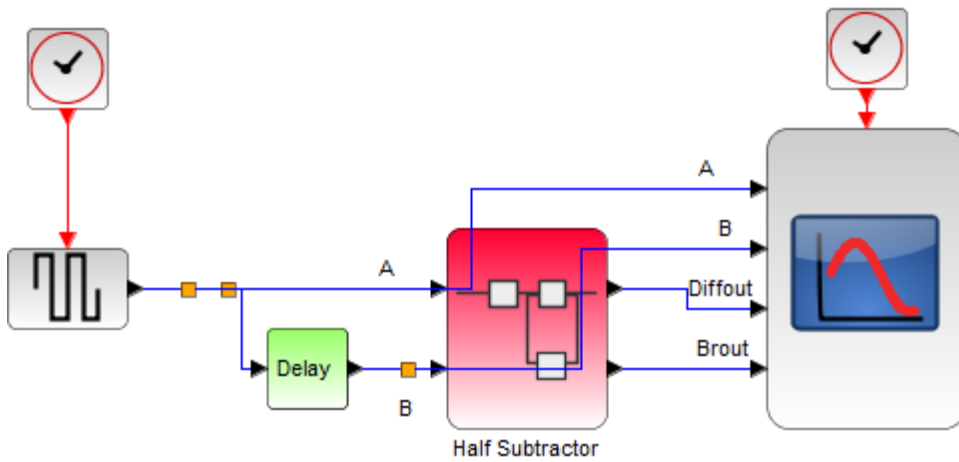


Figure 3.2: Half Subtractor design

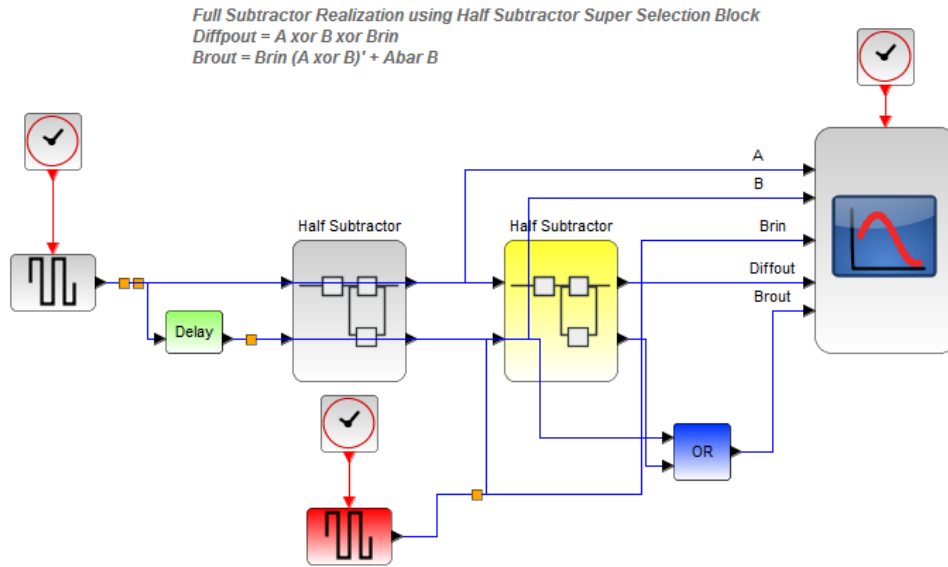

Note : Superselection of superselection not supported in Scilab Xcos.

Figure 3.3: Full Subtractor Design



Figure 3.4: Full Subtractor Design

## **Experiment: 4**

# **4 bit Ripple Carry Adder Design & Implementation in Xcos**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

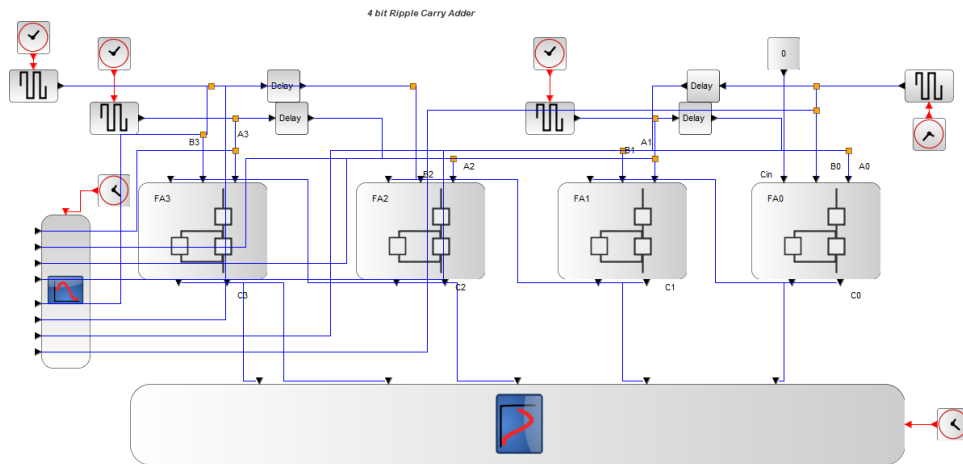


Figure 4.1: Ripple Carry Adder Design

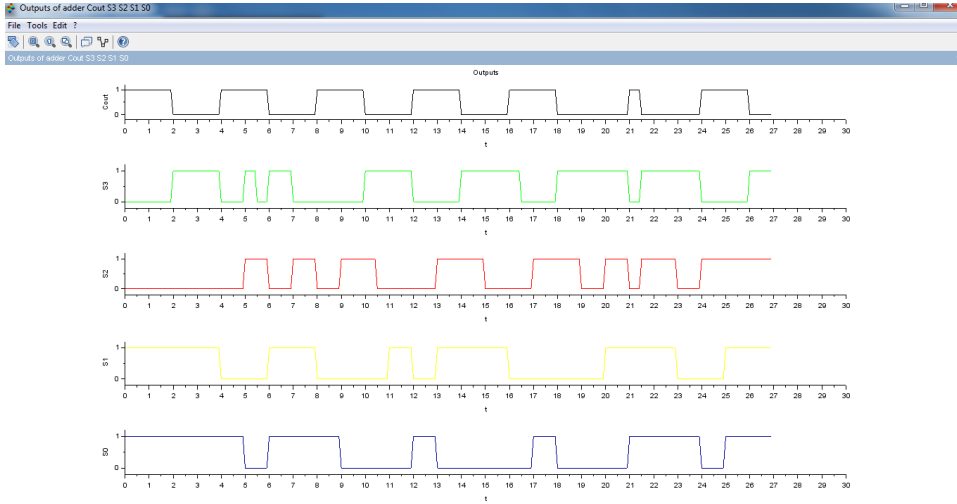


Figure 4.2: Ripple Carry Adder Design

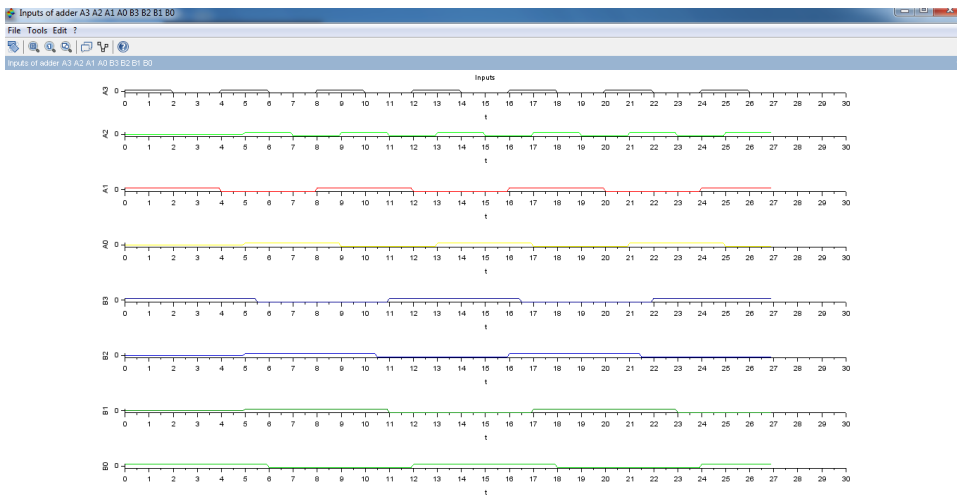


Figure 4.3: Ripple Carry Adder Design

## **Experiment: 5**

# **BCD Adder Design & Implementation in Xcos**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

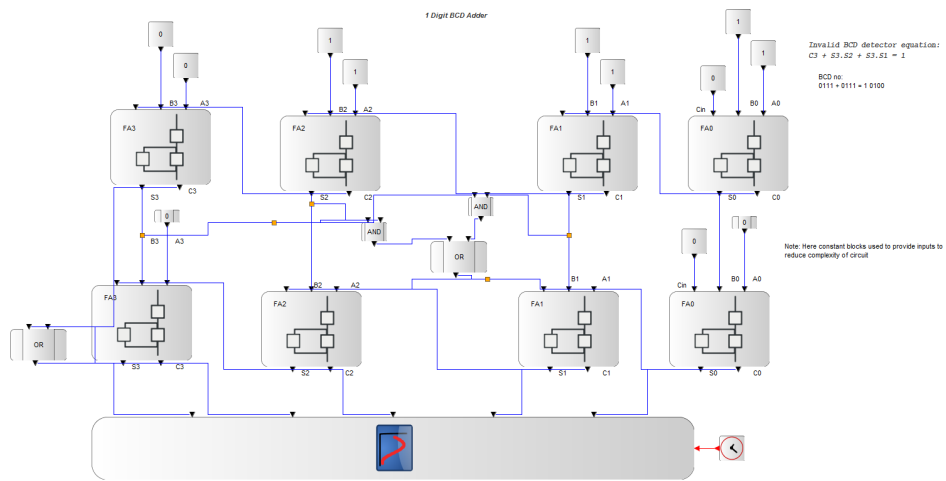


Figure 5.1: BCD Adder Design

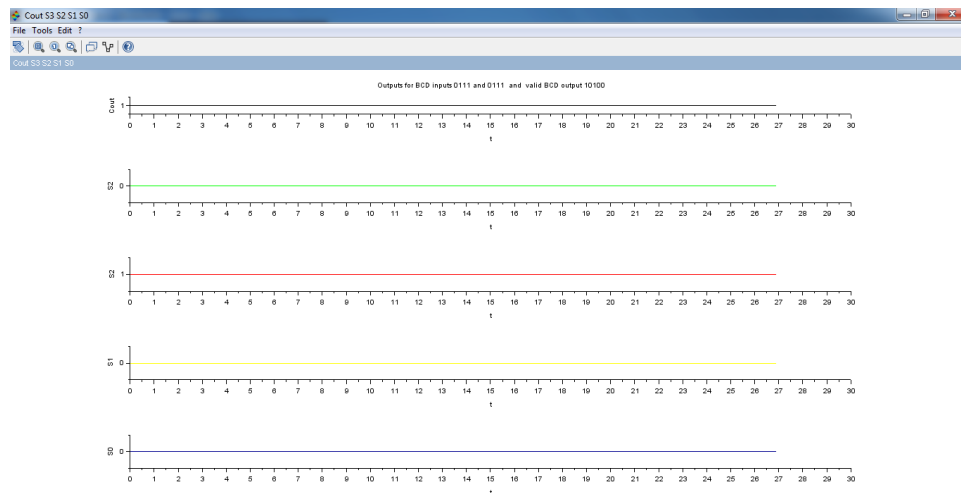


Figure 5.2: BCD Adder Design

## **Experiment: 6**

# **Multiplexer Design and implementation & its application in Xcos**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

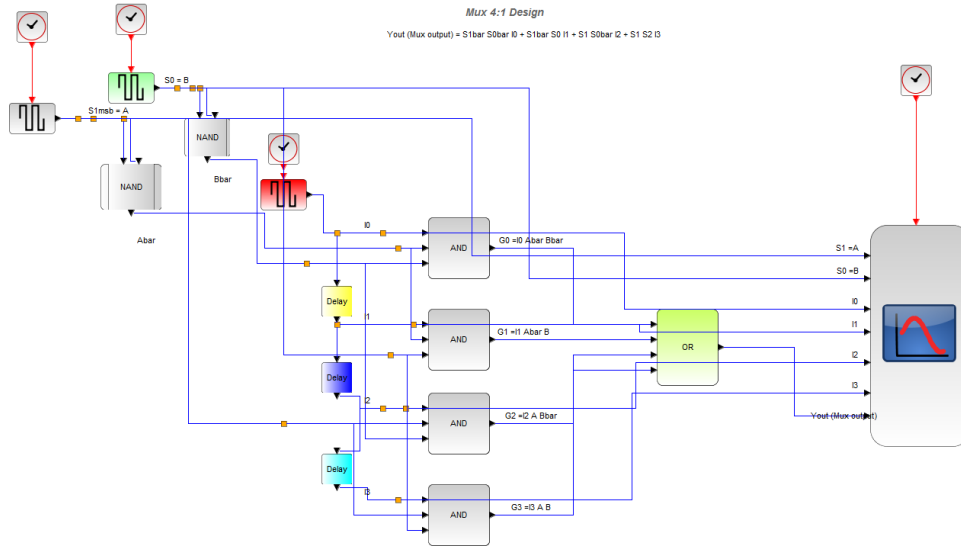


Figure 6.1: Multiplexer 4 to 1 design

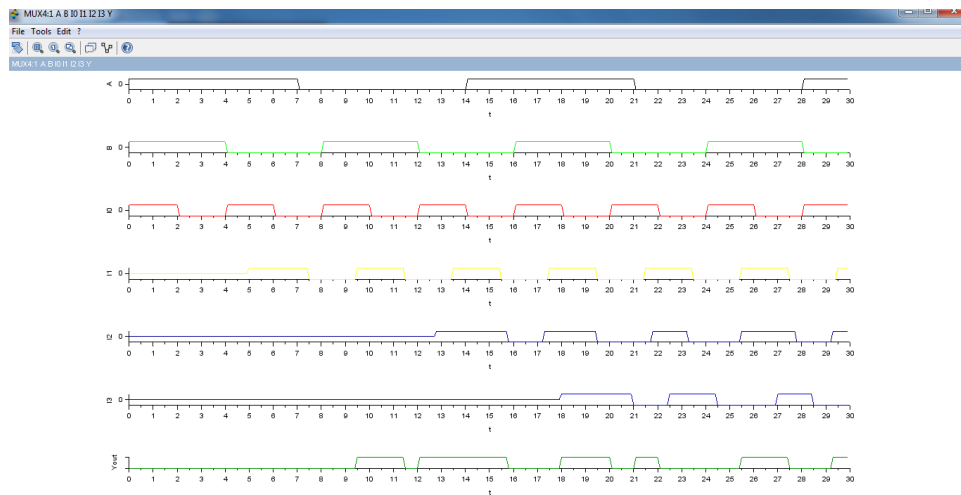


Figure 6.2: Multiplexer 4 to 1 design

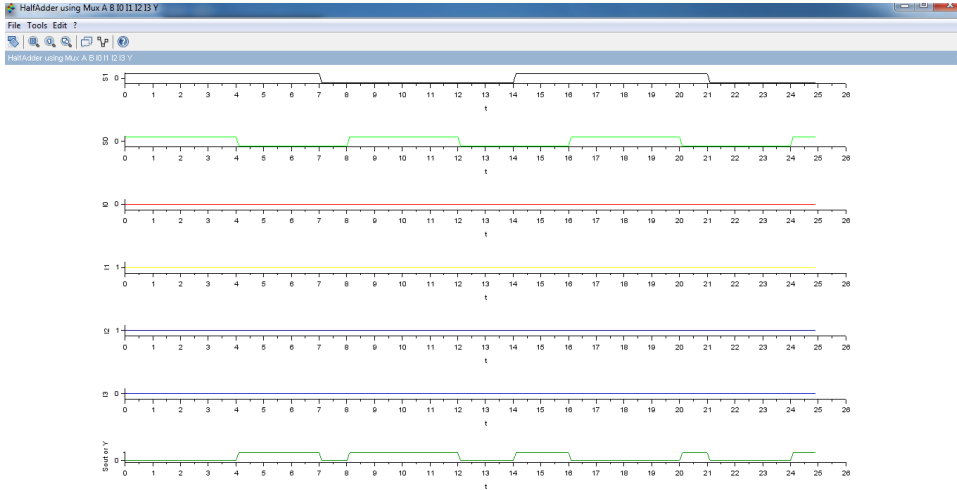


Figure 6.3: Multiplexer Application Half Adder design

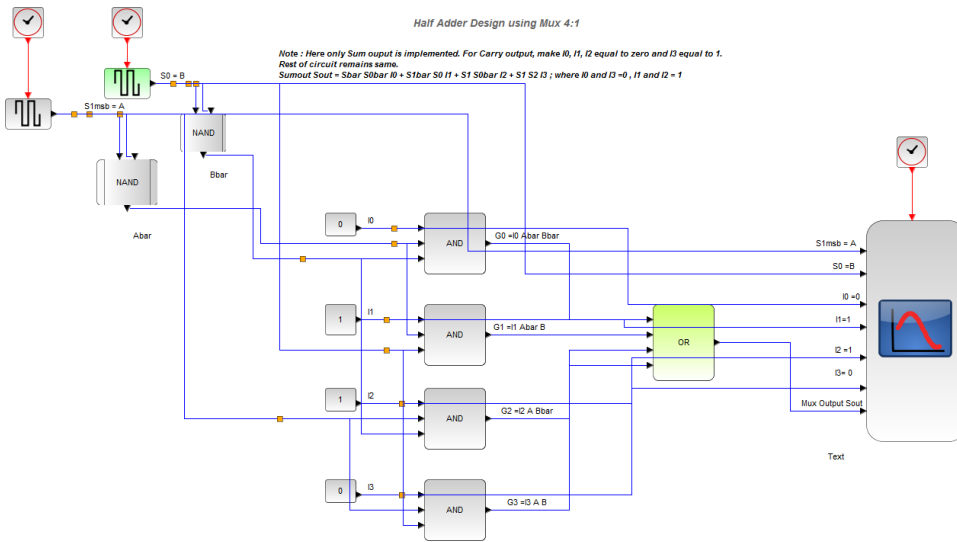


Figure 6.4: Multiplexer Application Half Adder design

## **Experiment: 7**

# **Demultiplexer Design and implementation & its application in Xcos**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

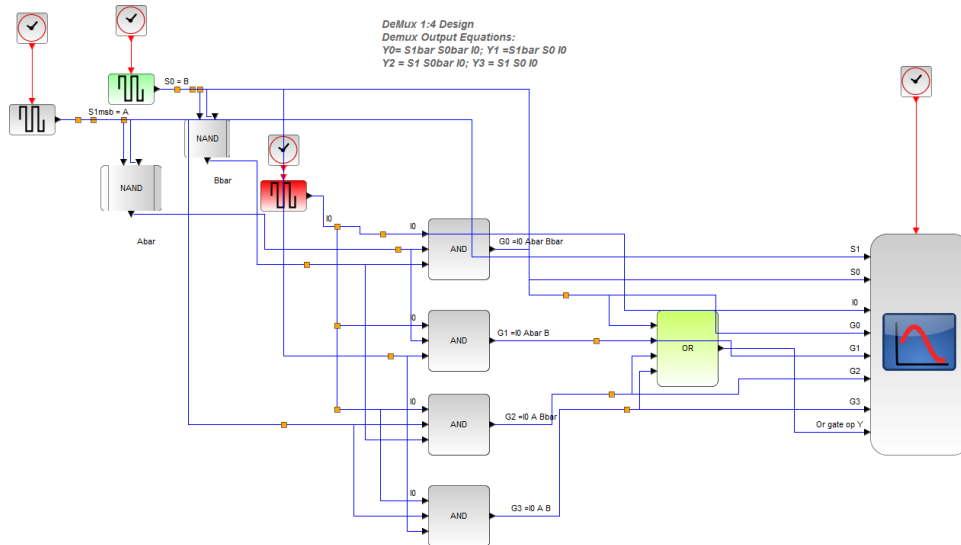


Figure 7.1: Demultiplexer 1 to 4

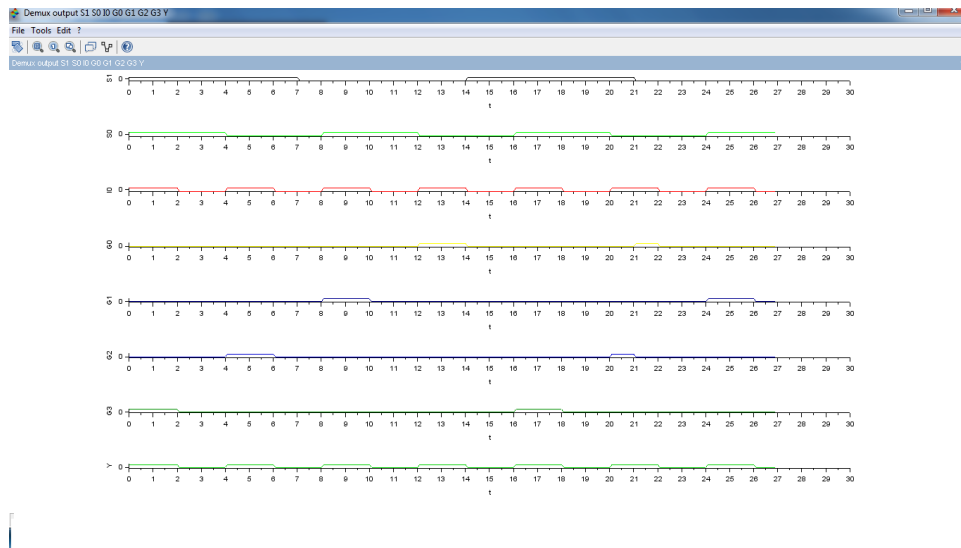


Figure 7.2: Demultiplexer 1 to 4

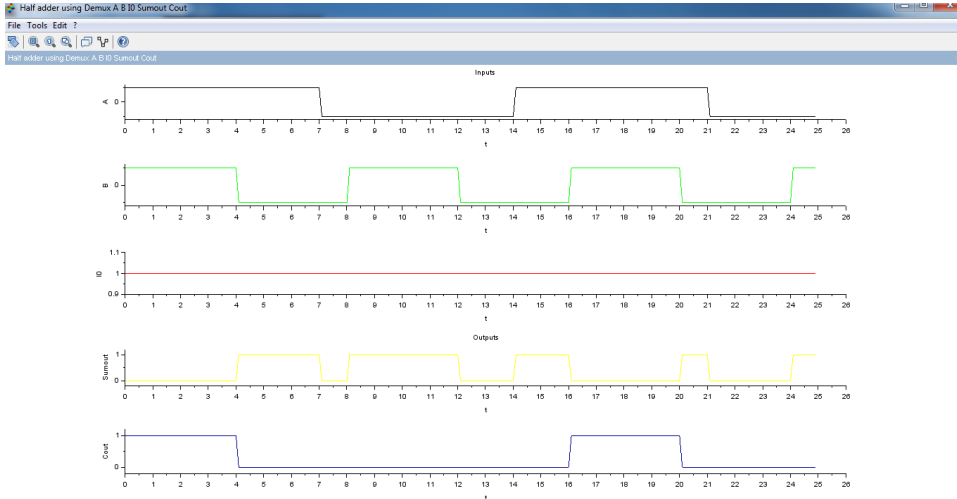


Figure 7.3: Demultiplexer Application Half Adder design

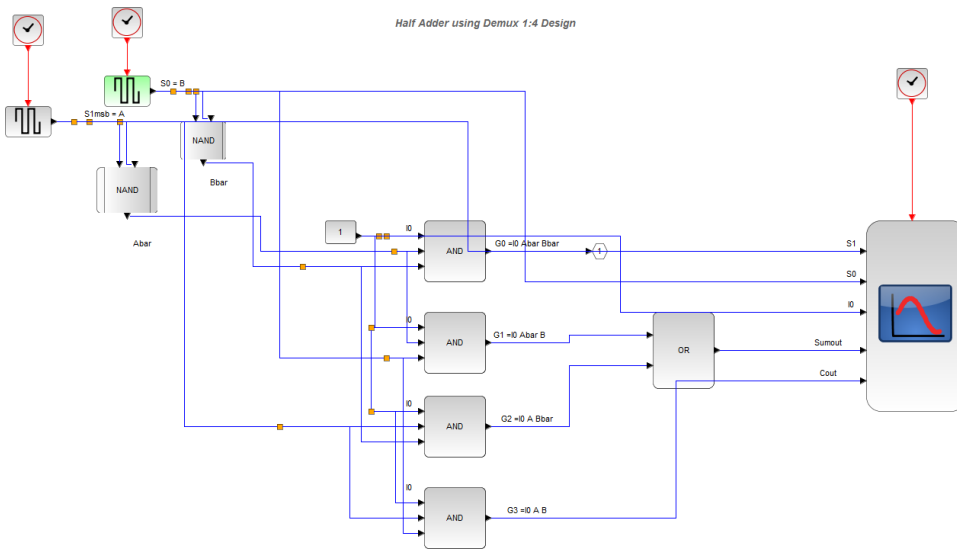


Figure 7.4: Demultiplexer Application Half Adder design

## **Experiment: 8**

# **Decoder Design and implementation & its application in Xcos**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

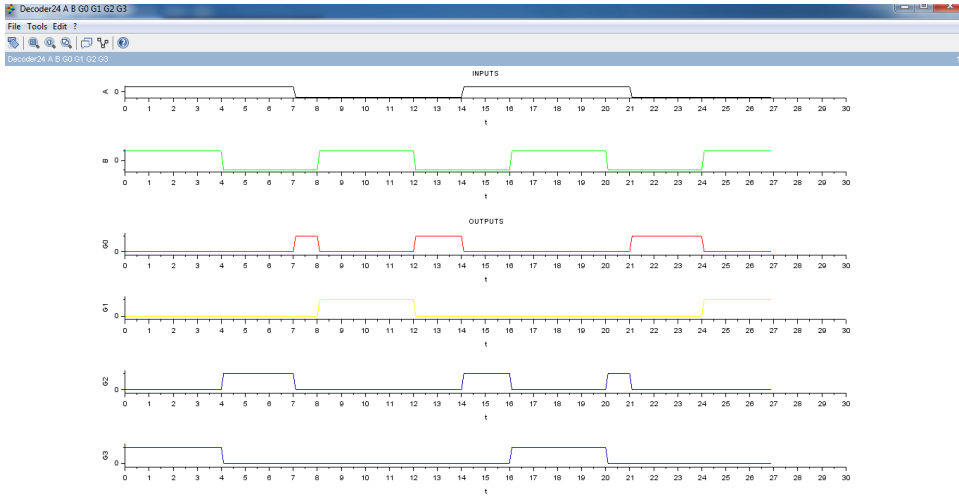


Figure 8.1: Decoder 2 to 4 design

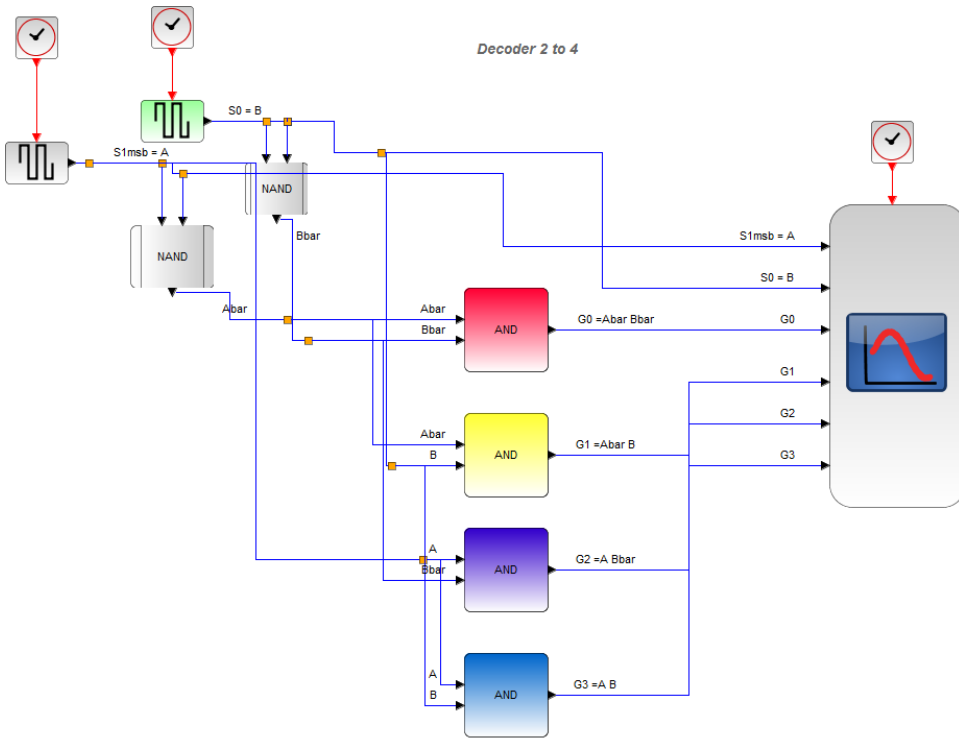


Figure 8.2: Decoder 2 to 4 design

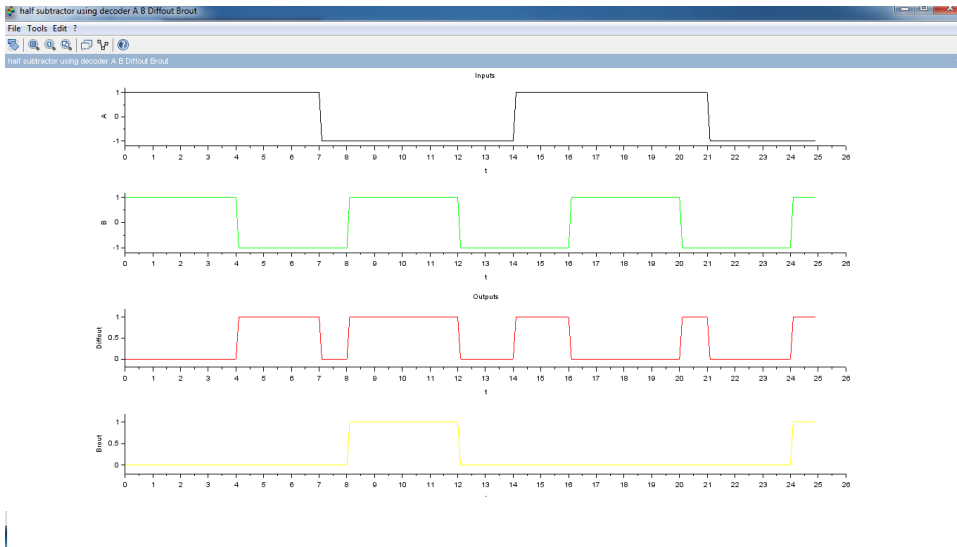


Figure 8.3: Decoder Application Half Subtractor design

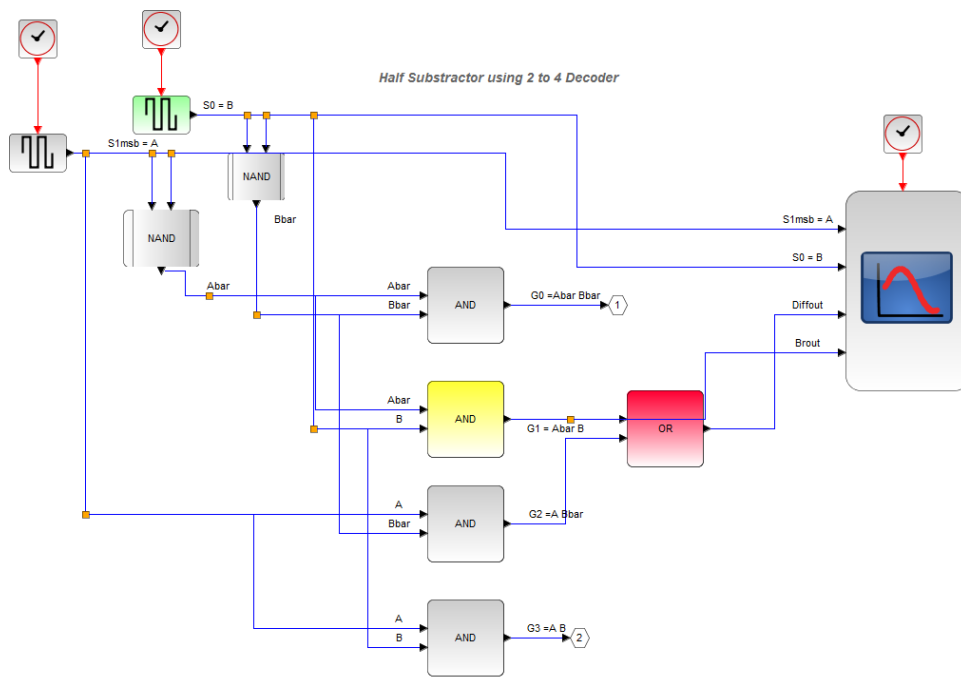


Figure 8.4: Decoder Application Half Subtractor design

## **Experiment: 9**

# **Flip flop Design & Implementation in Xcos**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

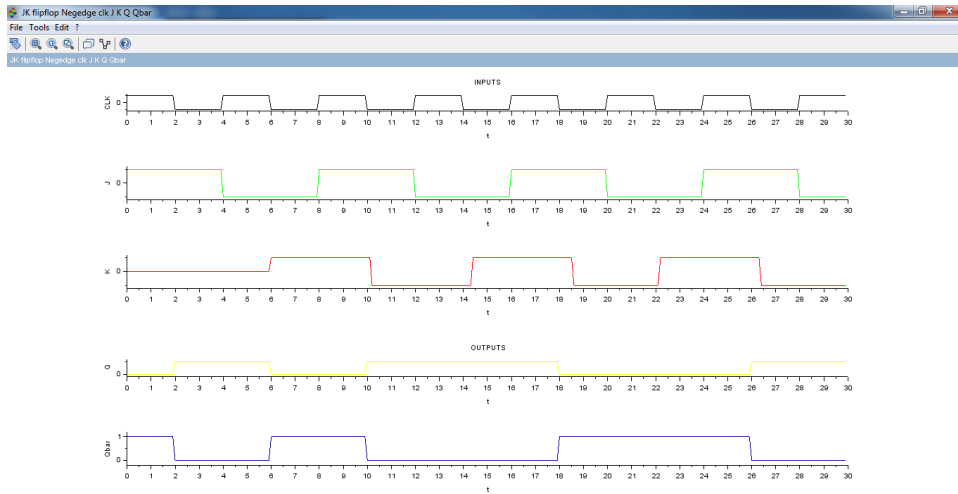


Figure 9.1: JK flip flop

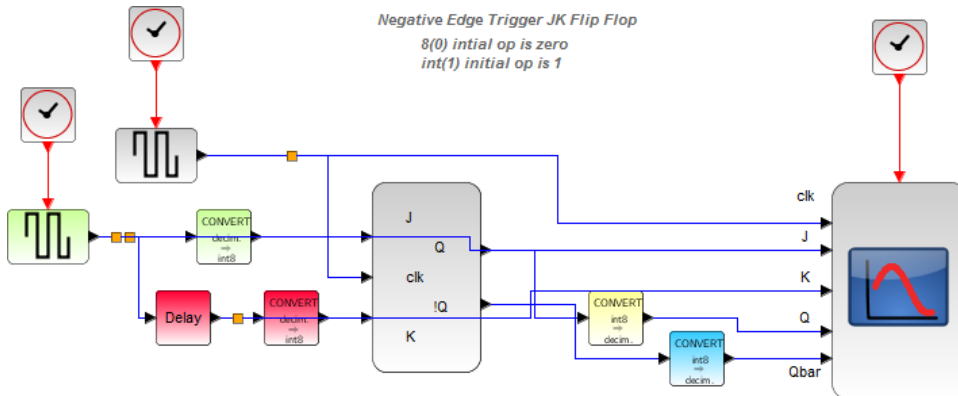


Figure 9.2: JK flip flop

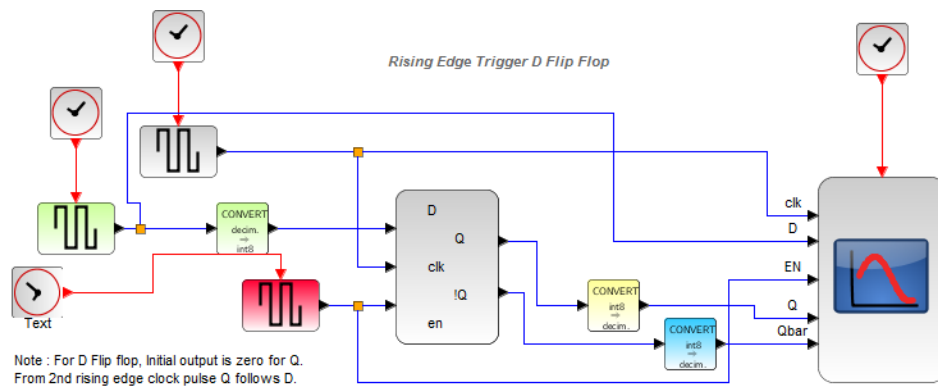


Figure 9.3: D flip flop

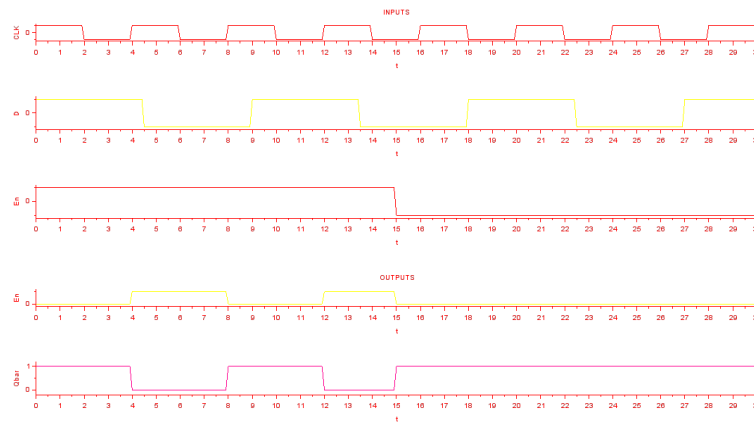


Figure 9.4: D flip flop

## **Experiment: 10**

# **Asynchronous Counter Design & Implementation in Xcos**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

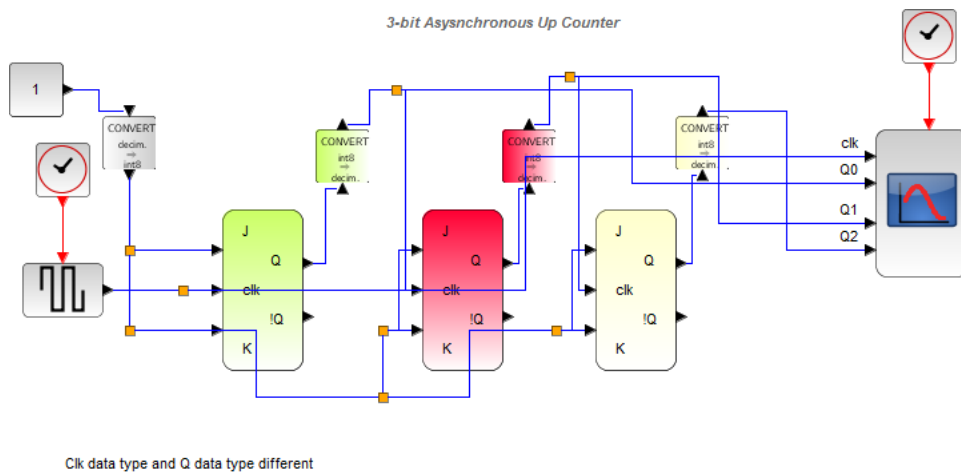


Figure 10.1: Asynchronous 3 bit up counter design

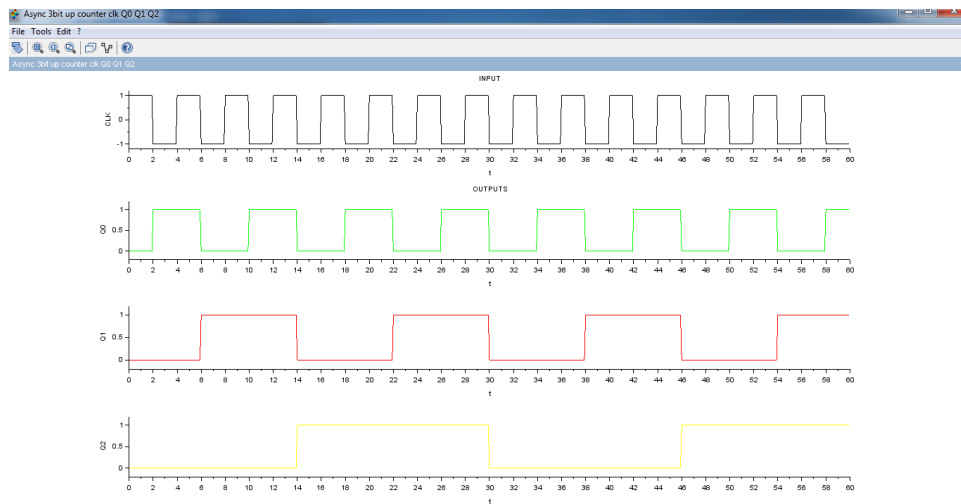


Figure 10.2: Asynchronous 3 bit up counter design

## **Experiment: 11**

# **Synchronous Counter Design & Implementation in Xcos**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

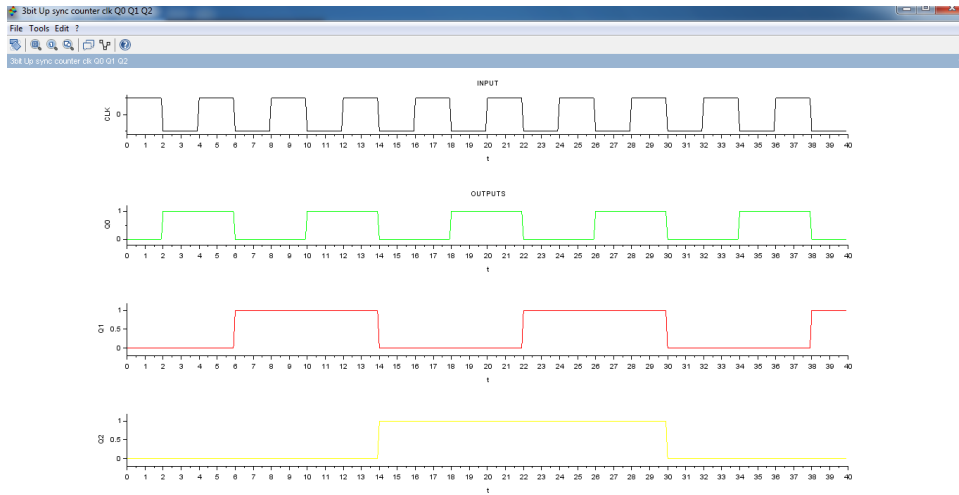


Figure 11.1: Three bit up synchronous counter

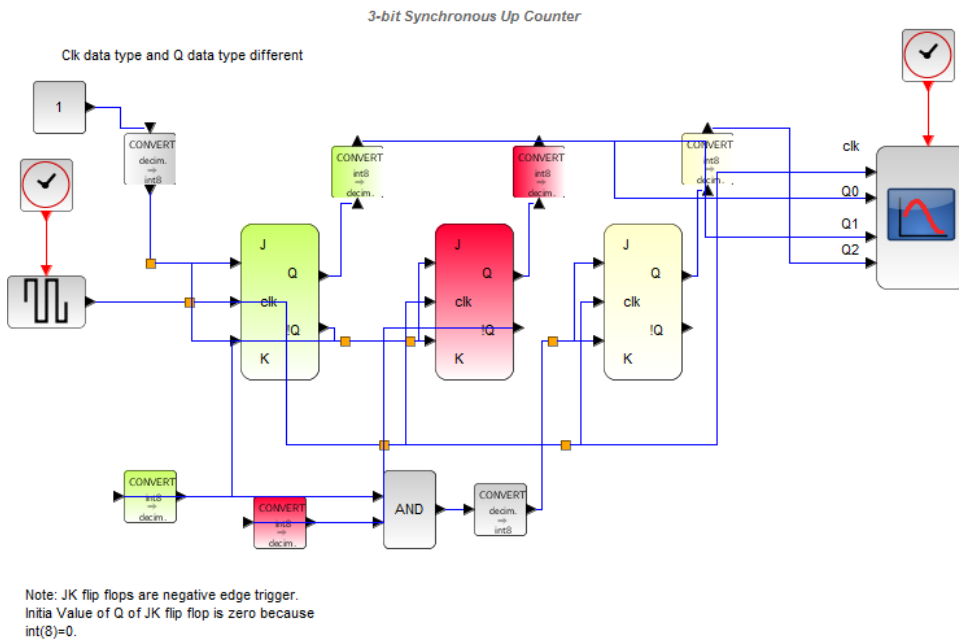


Figure 11.2: Three bit up synchronous counter

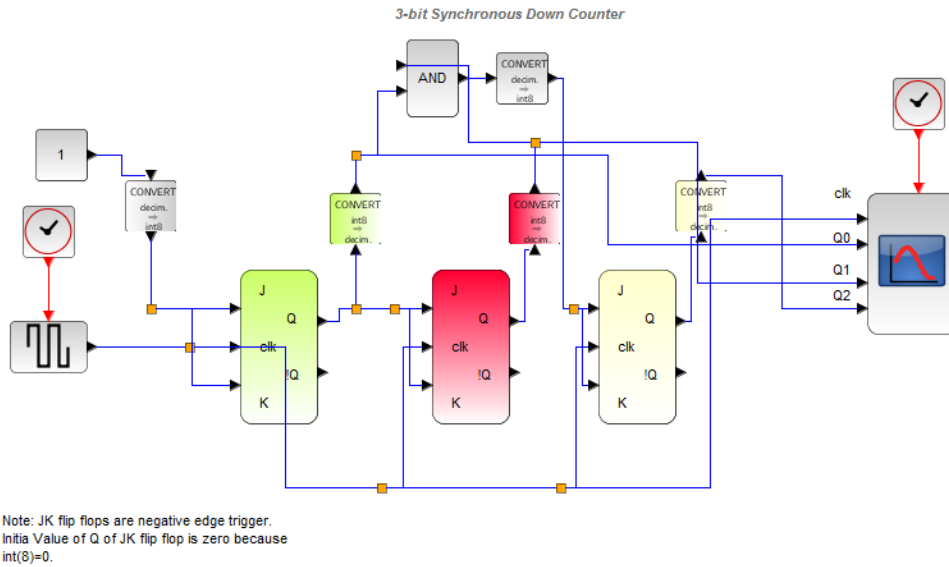


Figure 11.3: Three bit down synchronous counter

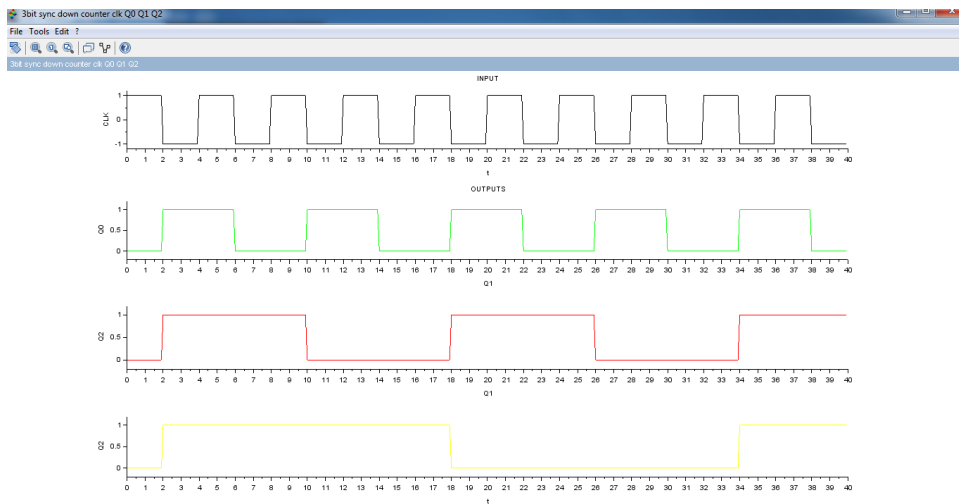


Figure 11.4: Three bit down synchronous counter

## **Experiment: 12**

### **Code Converter Design (eg.binary to gray code conversion) & Implementation in Xcos**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

Code Converter : 4 bit Binary to 4 bit Gray

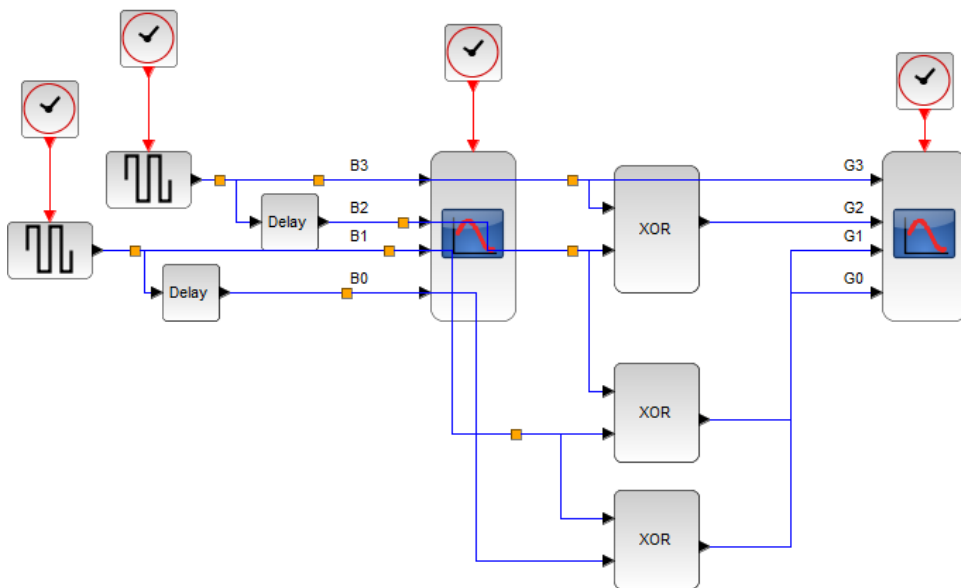


Figure 12.1: Binary to Gray code converter

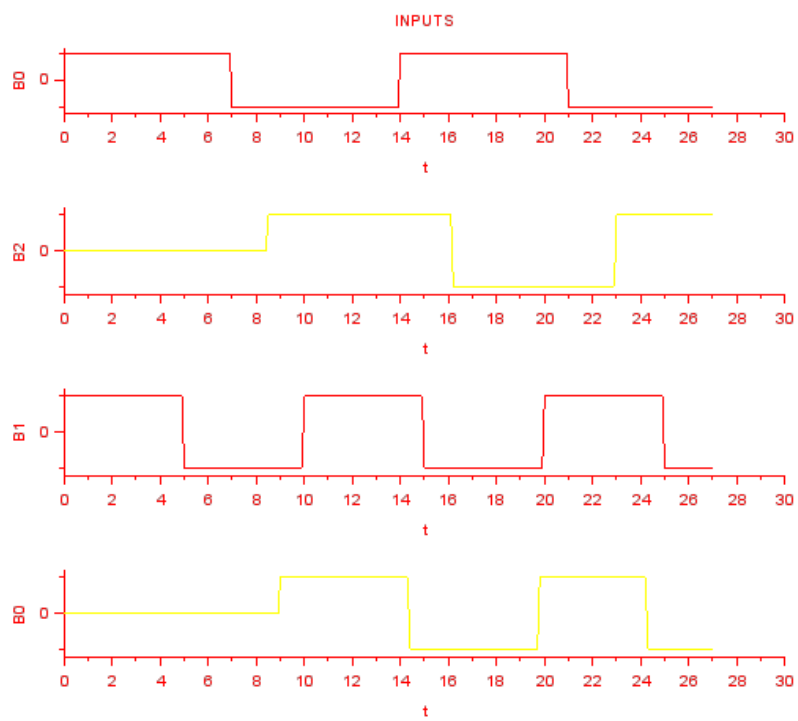


Figure 12.2: Binary to Gray code converter

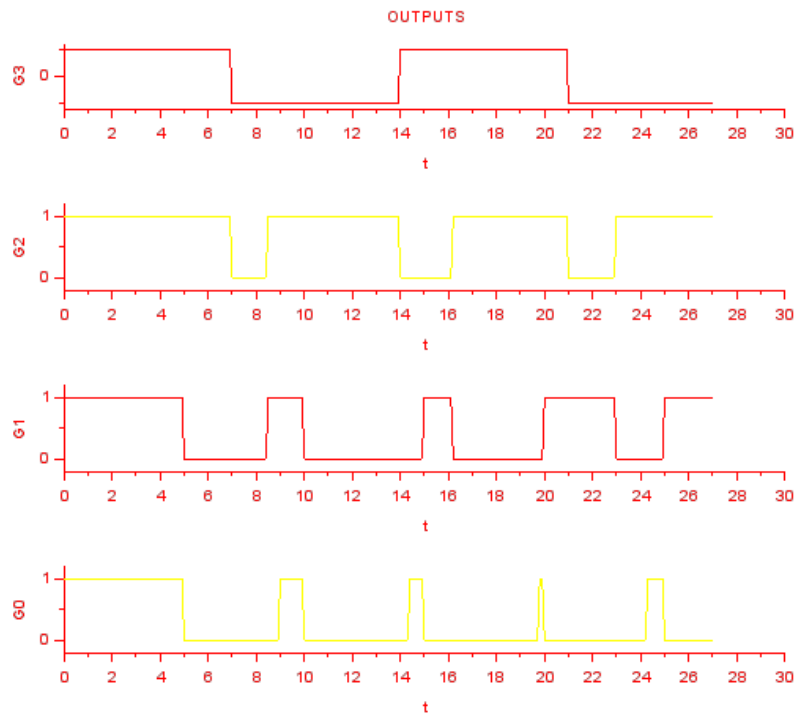


Figure 12.3: Binary to Gray code converter

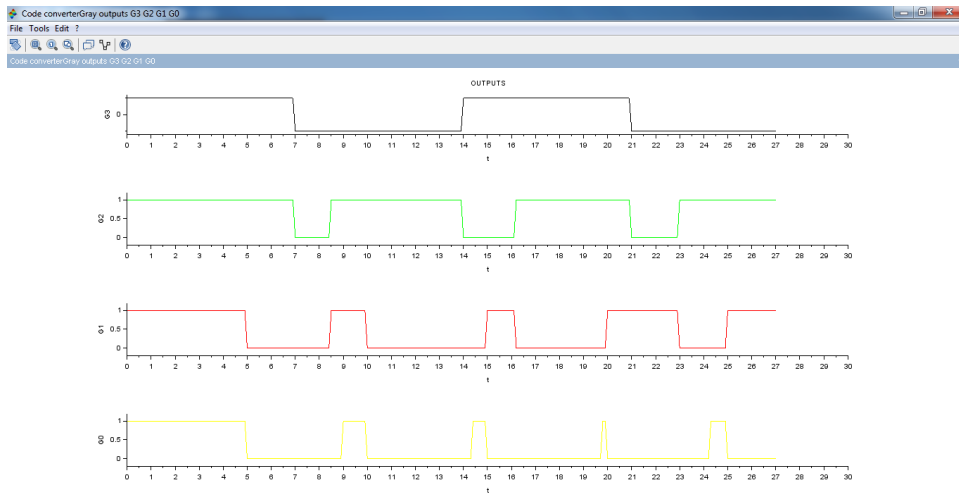


Figure 12.4: Binary to Gray code converter